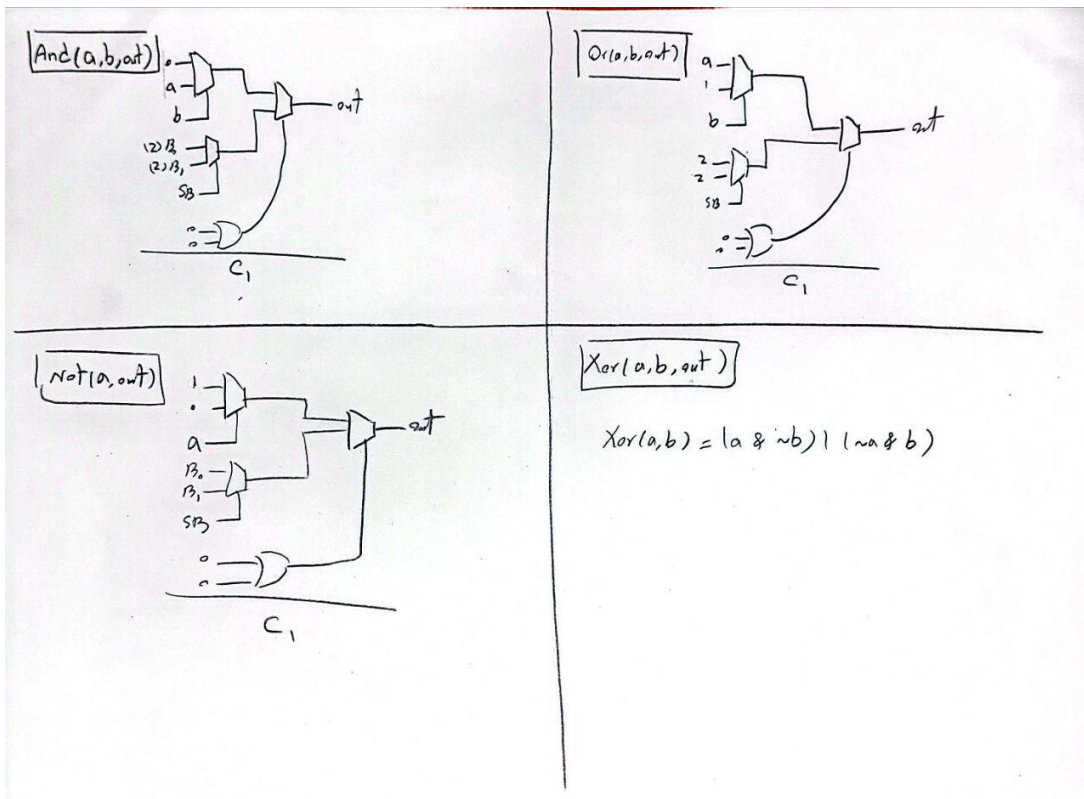


CAD - CA2

Mohammad Amanlou: 810100084


Shahzad Momayez: 810100272

At first, after defining the given basic structures, with a little thought, we defined the basic Verilog gates like and or not.




Then we defined a base register as follows:


Register (a, clk, rst, en, out)

 


1. Datapath:

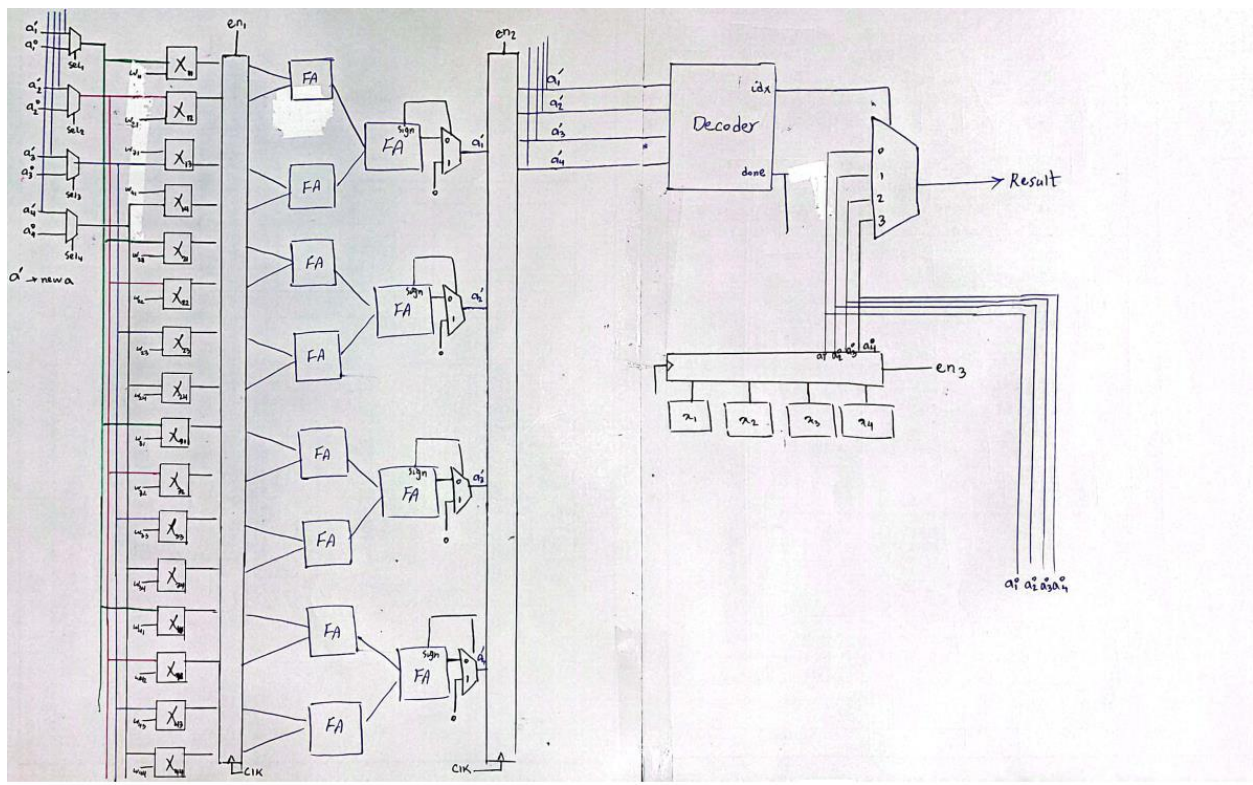

 1.1. Adder: we have used a 5 bit Ripple Carry Adder




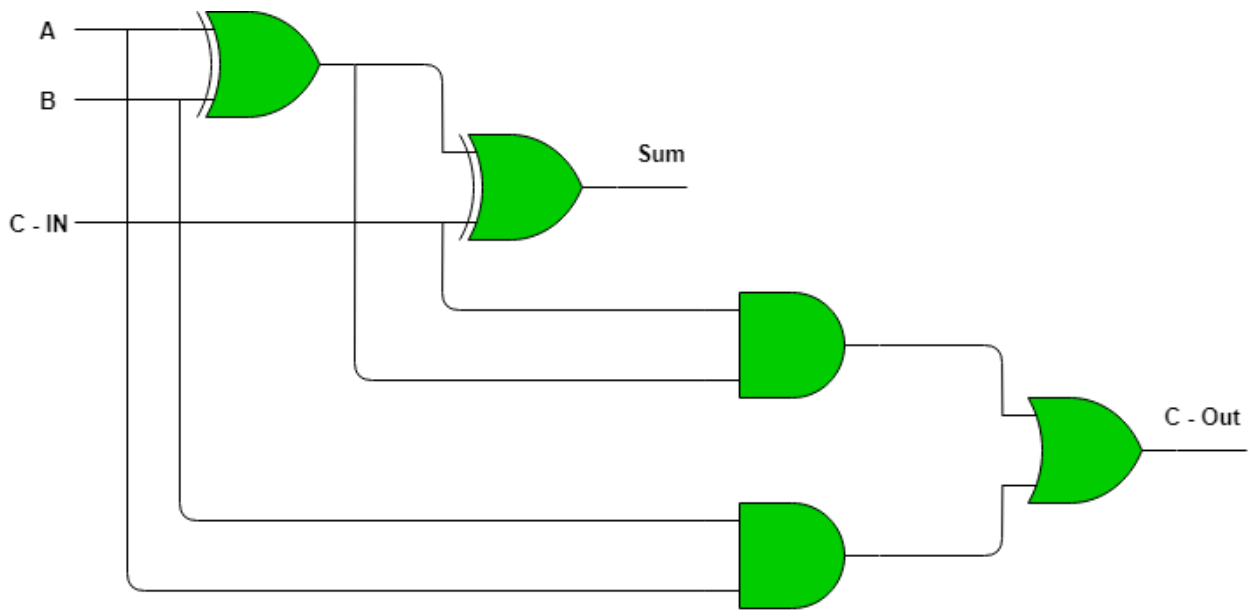1.1.1. FA: we have used this formation of FA using XOR and AND and OR gates




1.2. Multiplier:

2's Complement Multiplier

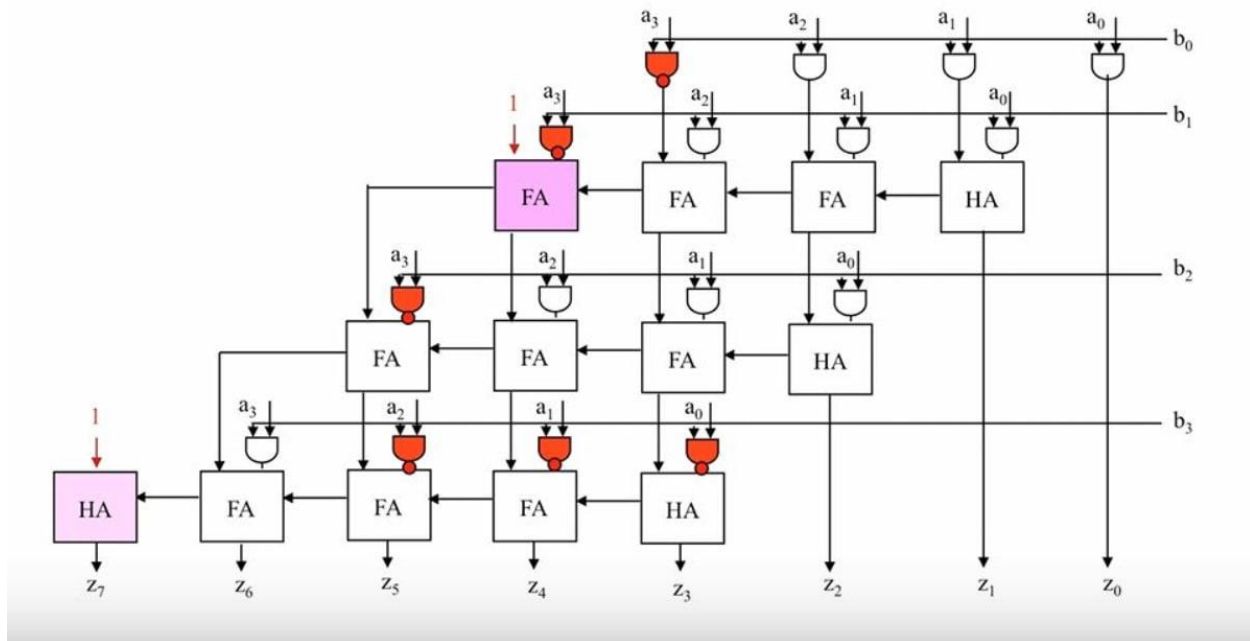

- 1.3. Decoder:** First, we define an adder module to convert a 5-bit number to a 1-bit zero or one. Then we convert each number to a value of zero or one. Then, with some thought (a better way is to draw the Karnaugh map, which is omitted here for simplicity), we arrive at the following equation.
- $$\text{done} = A1A2A3A4' + A1A2A3'A4 + A1A2'A3A4 + A1'A2A3A4$$
- $$\text{idx} = \{A1A2, A1A3\}$$

2. Controller:

 

2.1. Transition table:

A	B	C	start	done	A ⁺	B ⁺	C ⁺	en3	en2	en3	sel
0	0	0	0	-	0	0	0	-	0	1	-
0	0	0	1	-	0	0	1	-	0	1	-
0	0	1	-	-	0	1	0	1	-	-	1
0	1	0	-	-	1	0	0	-	1	-	-
1	0	0	-	0	0	1	1	-	-	-	-
1	0	0	-	1	1	0	1	-	-	-	-
0	1	1	-	-	0	1	0	1	-	-	-
1	0	1	-	-	0	0	0	-	-	1	-

P4PCO

2.2. Boolean algebra:

Subject.

Date.

$$A^+ = \bar{A}B\bar{C} + A\bar{B}\bar{C} \text{ Done}$$

$$B^+ = \bar{A}C + A\bar{B}\bar{C} \text{ Done}$$

$$C^+ = \bar{B}\bar{C} \text{ start} + A\bar{B}\bar{C}$$

$$en1 = \bar{A}C$$

$$en2 = \bar{A}B\bar{C}$$

$$en3 = \bar{A}\bar{B}\bar{C}$$

$$sel = \bar{A}\bar{B}C$$